

JSA - 1

KEY ANSWERS

i) a)  $\left(\frac{W}{L}\right)_{1,2} = \frac{25}{0.5}$ ,  $V_{RSS} = 0.6V$

$$m_n C_{ox} = 50 \mu A/V^2$$

$$V_{th} = 0.5V$$

$$\lambda = \gamma = 0$$

$$V_{DD} = 3V$$

i)  $V_{in} = V_{cm(min)}$

$$= V_{GS1} + V_{RSS} \quad \text{--- (1)}$$

$$I_D = m_n C_{ox} \left(\frac{W}{L}\right)_1 \frac{(V_{GS1} - V_t)^2}{2}$$

$$\frac{1mA}{2} = 50 \times 10^{-6} \times \frac{25}{0.5} \times \frac{(V_{GS1} - 0.5)^2}{2}$$

$$0.5 \times 10^{-3} = 50 \times 10^{-6} \times 50 \times \frac{(V_{GS1} - 0.5)^2}{2}$$

$$4 \times 10^{-4} \times 10^{-3} \times 10^{16} = (V_{GS1} - 0.5)^2$$

$$0.4 = (V_{GS1} - 0.5)^2$$

$$V_{GS1} - 0.5 = 0.632V$$

$V_{GS1} = 1.132V$

$$V_{cm(min)} = 1.132 + 0.6 \quad (\text{from eq. (1)})$$


$V_{cm(min)} = 1.732V$

ii)  $R_D = ?$  diff. gain = 5

$$\rightarrow A_d = g_m R_{DS} \Rightarrow g_m = \frac{2 I_D}{V_{ov}}$$

$$\rightarrow g_m = \frac{2 \times 0.5 \times 10^{-3}}{1.132 - 0.5} = 1.58 \times 10^{-3} \Rightarrow R_D = \frac{5}{1.58 \times 10^{-3}}$$

$R_D = 3.164 k\Omega$

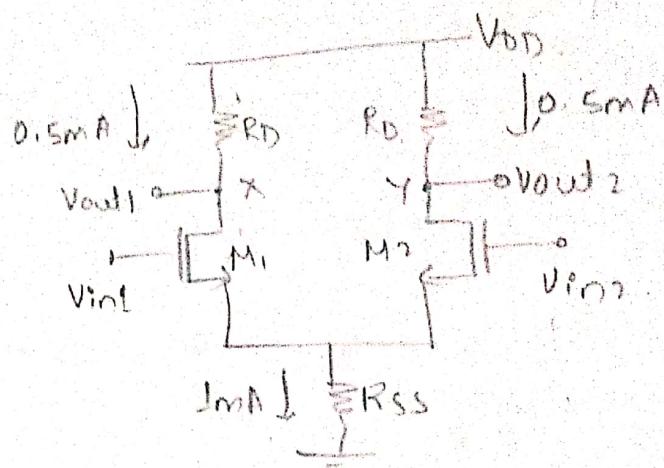

$$\text{Q6. } \left(\frac{w}{l}\right)_{1,3} = \frac{5\mu}{0.18\mu}$$

$$m_{nCOX} = 100 \mu A/V^2$$

$$V_t = 0.5 V$$

$$I = 0.5 \text{ mA}$$

$$I = m_{nCOX} \left(\frac{w}{l}\right) \frac{(V_{GS} - V_t)^2}{2}$$

$$0.5 \times 10^{-3} = 100 \times 10^{-6} \times \frac{5}{0.18} \times \frac{1}{2} (V_{GS} - 0.5)^2$$

$$0.36 = (V_{GS} - 0.5)^2 \Rightarrow V_{GS} - V_t = 0.6 = V_{DS(\min)}_2$$

$$V_{GS} = 1.1 V$$

$$V_b = 2 V_{GS} \quad (V_{GS3} + V_{GS2}) = (2 V_{GS})$$


$$V_b = 2 \times 1.1$$

$$V_b = 2.2 V$$

$$\text{OR } V_b = V_{GS}(M3) + V_{DS(\min)}_2$$

$$V_b = 1.1 + 0.6$$



$$V_b = 1.7 V$$

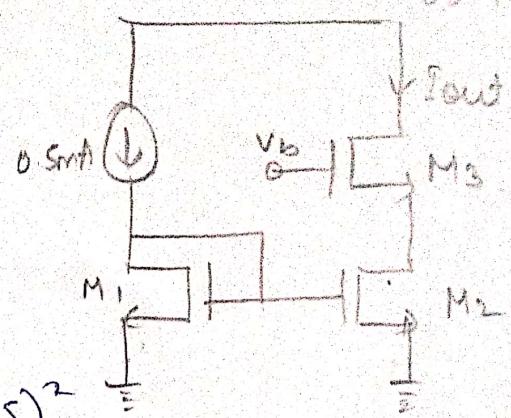
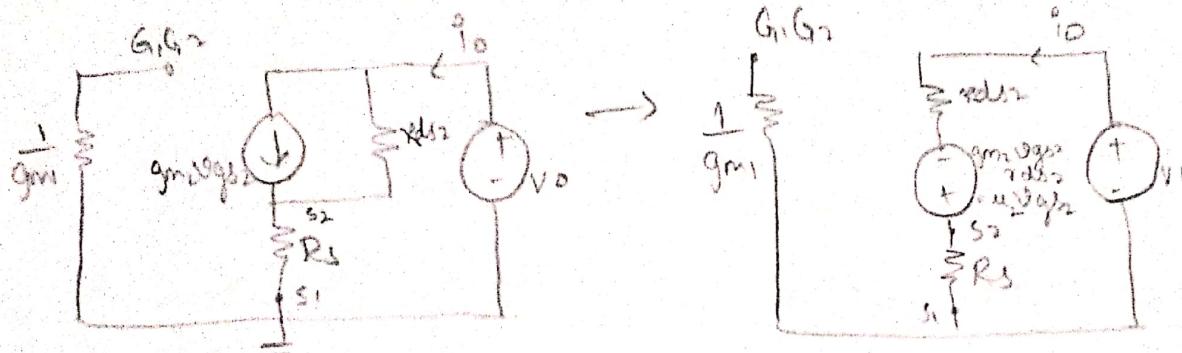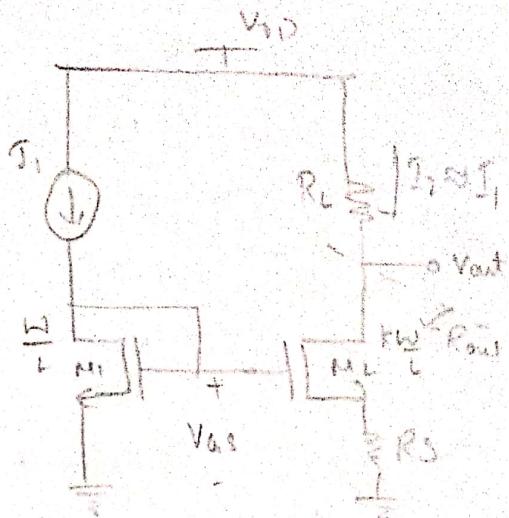
### 1) c) Widlar current mirror.

→ To improve performance parameter or the output resistance, we have to flatten the curve by increasing size of  $M_2$  (increasing length) but the topological approach is to attach  $R_s$  at the source terminal.

- For better current mirror high op resistor is must.



$$\rightarrow V_{g1} = V_{g2} = V_{S1} = 0$$

$$\rightarrow V_{S2} = i_o R_{ds}$$

$$\rightarrow V_{g2} = 0 - i_o R_s = -i_o R_s$$

$$\begin{aligned} \rightarrow \text{KVL to the loop} & \Rightarrow V_o - i_o r_{ds2} + \mu_2 V_{g2} - i_o R_s = 0 \\ & = V_o - i_o r_{ds2} - \mu_2 i_o R_s - i_o R_s = 0 \end{aligned}$$

$$\therefore V_o = i_o (r_{ds2} + R_s + \mu_2 R_s)$$

considering all  $r_{ds} = r_{ds}$ .




$$\therefore R_o = \frac{V_o}{i_o} = r_{ds} + R_s + \mu_2 R_s = \boxed{r_{ds} + (\mu + 1) R_s}$$

- If  $R_s$  inc,  $\bar{I}_2 R_s$  inc. terminal voltage of  $M_2$  dec. i.e.  $V_{DS}$  decreases, current reduces so voltage drop across  $R_s$  also decreases. So  $V_{GS}$  tends to increase.
- Effectively  $R_o$  is increased. (by  $(1+\mu) R_s$ ).

To increase the output resistance
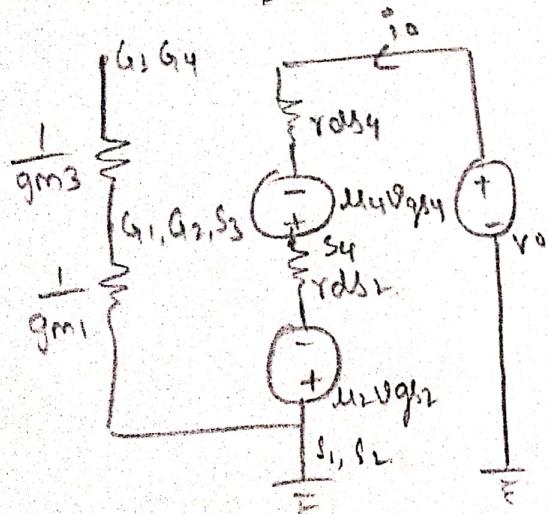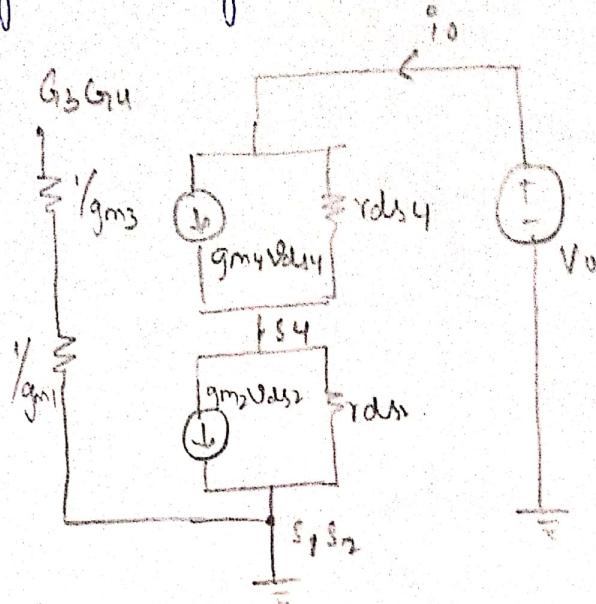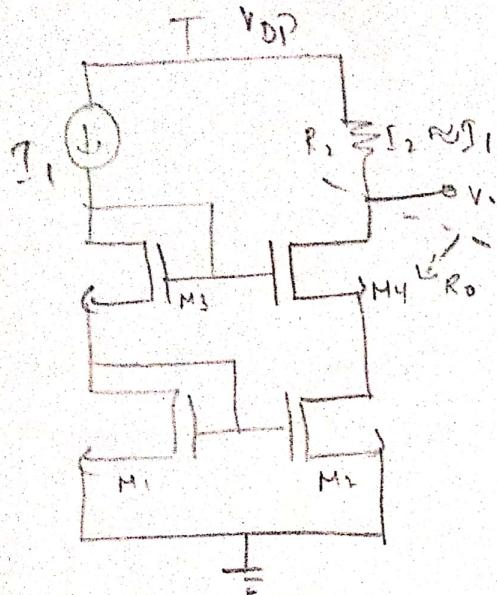
## Cas code current mirror.

Source resistance replaced by current mirror.



$$V_{S1} = V_{S2} = 0.$$

$$Vg_1 = Vg_2 = Vg_3 = Vg_4 = 0.$$

$$V_{xy} = i_0 r ds z + M_2 V g s^2$$

$$V_{S4} = \text{Polaris 2}$$

$$U_{Q_8} = -i \sigma_2.$$

$$V_0 - i_1 rds_1 + M_1 Vgs_1 - i_2 rds_2 + M_2 Vgs_2 = 0$$

$$v_0 - 10 \text{ m/s} - 2 \times 4 \text{ m/s} = 0$$

$$V_0 = R_0 \cdot rds_4 + M_0 rds_4 + rods^2$$

$$= r_{ds2} = r_{ds4} = r_{ds} \quad (\text{Because all } gm \text{ are same})$$

$$\frac{V_0}{g} \cdot R_0 = 2r \text{ rods} + 114 \text{ rods}$$

Therefore output resistance is

$$R_o = (\alpha + \mu) r_{ds}$$

If  $r_{ds} = 100\text{k}\Omega$

$$g_m = 1\text{mA/V}$$

$$\mu = g_m r_{ds}$$

$$\mu = 100$$

$$R_o = (\alpha + 100) r_{ds}$$

$$\approx (102)(100)\text{k}$$

$$\approx 10200\text{k}$$

$$R_o = 10.2\text{M}\Omega$$

Hence the output resistance is increased by 100 times.

$$2a) \frac{W}{L} = 2.$$

$$V_{DD} = 2V$$

$$m_{n\text{ox}} = 100 \mu\text{A/V}^2$$

$$V_{th} = 0.5V.$$

Considering MOSFET as in sat. region.

$$I_{DS} = \frac{1}{2} m_{n\text{ox}} \frac{W}{L} (V_{GS} - V_t)^2.$$

$$\frac{2 - V_{out}}{10 \times 10^3} = \frac{1}{2} \times 100 \times 10^{-6} \times 2 \times (V_{in} - 0.5)^2$$

$$2 - V_{out} = (V_{in} - 0.5)^2$$

$$V_{in} = V_{GS}.$$

$$V_{out} = V_{DS}.$$

$$2 - V_{DS} = (V_{GS} - 0.5)^2.$$

Transistor switches from Sat. to linear region when  
 $V_{DS} < V_{GS} < V_t$ .

$$= V_{DS} = 2 - (V_{GS} - 0.5)^2$$

$$= 2 - (V_{GS} - 0.5)^2 < V_{GS} - 0.5.$$

$$\text{let } (V_{GS} - 0.5) = x$$

$$= 2 - x^2 < x.$$

$$= x^2 + x - 2 > 0.$$

$$= (x+2)(x-1) > 0$$

$$= (x+2) > 0 \text{ } \& \text{ } (x-1) > 0 \text{ or } (x+2) < 0 \text{ } \& \text{ } (x-1) < 0.$$

considering  $x > 1$ :

$$x-1 > 0 \text{ } \& \text{ } x+2 > 0$$


$$x > 1 \text{ } \& \text{ } x > -2.$$

$$\Rightarrow V_{GS} - 0.5 > 1 \Rightarrow V_{GS} > 1.5V. \Rightarrow [V_{in} > 1.5V.] \text{ (Transition occurs)}$$


$$\Rightarrow I_{DS} = \frac{1}{2} \times 100 \times 10^{-6} \times 2(1.5 - 0.5)^2 \rightarrow [I_{DS} = 100 \mu\text{A}]$$

$$\Rightarrow V_{GS} = 1.5 - 0.5 = 1V. \Rightarrow V_{GS} > 1.5V \rightarrow \text{Saturation}$$

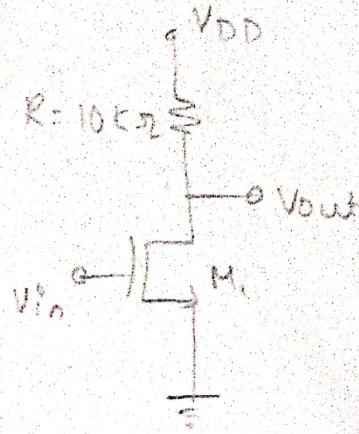
$$V_{GS} < 1.5V \rightarrow \text{Triode.}$$



Q b)

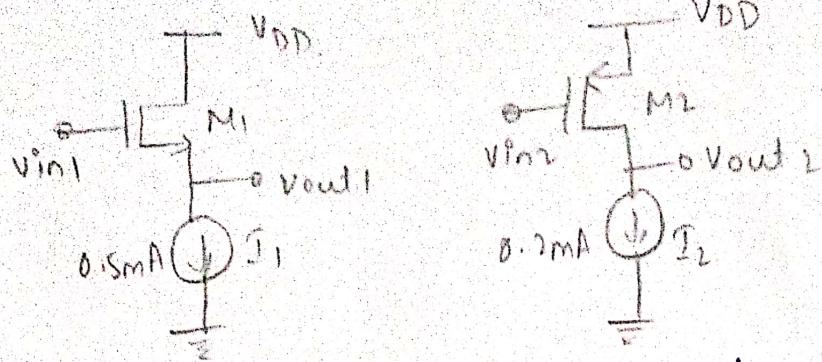

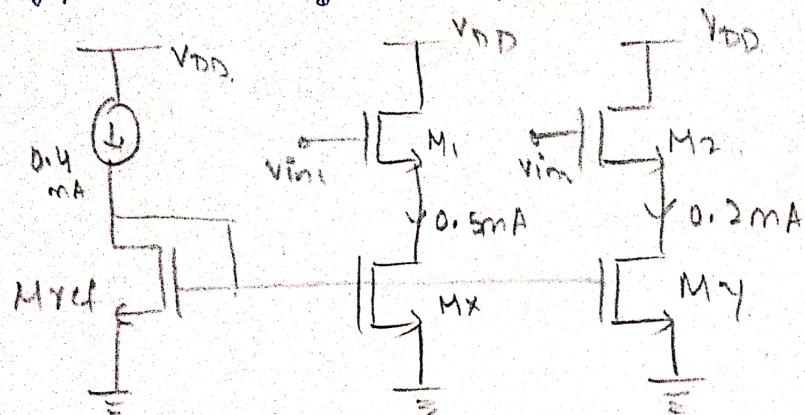→ Application of multiple current source.



$$\Rightarrow \text{WKT } \frac{I_{\text{out}}}{I_{\text{ref}}} = \frac{(\omega|L)_2}{(\omega|L)_1}$$


$$\Rightarrow \frac{I_2}{I_{\text{ref}}} = \frac{(\omega|L)_2}{(\omega|L)_{\text{ref}}}$$

$$= \boxed{\left( \frac{\omega}{L} \right)_2 = \left( \frac{5}{4} \right) \left( \frac{\omega}{L} \right)_{\text{ref}}}$$

$$\Rightarrow \frac{I_3}{I_{\text{ref}}} = \frac{(\omega|L)_y}{(\omega|L)_{\text{ref}}}$$

$$= \boxed{\left( \frac{\omega}{L} \right)_y = \left( \frac{1}{2} \right) \left( \frac{\omega}{L} \right)_{\text{ref}}}$$
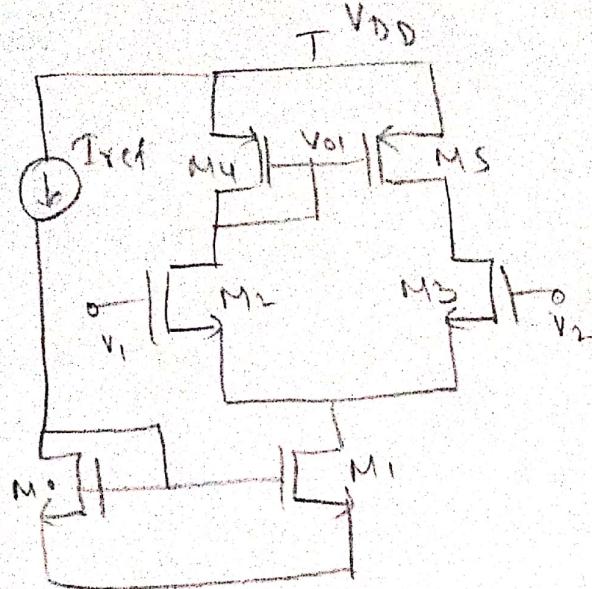
## 2) (c). 5-pack differential amplifier.



AC eq. ckt

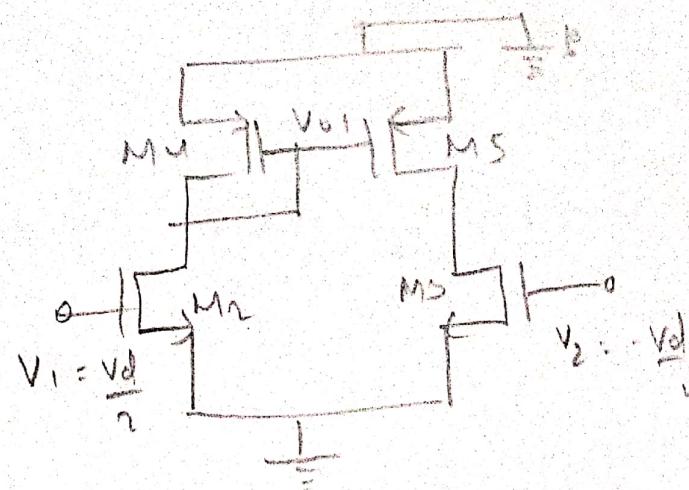


Fig-1 - M1 replacing tail resistance.

- Tails inc. CMRR.
- TT shared b/w M4 & M5.

Fig-2  $V_o = V_o' + V_o''$  — (1)

$V_o'$   $\rightarrow V_1$ ; path  $M_2 \rightarrow M_4 \rightarrow M_5$ . ( $V_1 \rightarrow V_{o1}, V_o'$ )

$V_o'' \rightarrow V_2$ ; path  $M_3 \rightarrow M_5$ .

- Network is not symmetric.

Case ①  $V_i = \frac{V_d}{2} = V_1 = V_o'$

$$V_{o1} = -g_{mn} (r_{dsn} \parallel 1/g_{mp}) \frac{V_d}{2} — (2)$$

$$V_o' = -g_{mp} (r_{dsp} \parallel r_{dsn}) V_{o1} — (3)$$

Put ② in ③

$$V_o' = g_{mp} g_{mp} (r_{dsn} \parallel 1/g_{mp}) (r_{dsp} \parallel r_{dsn}) \frac{V_d}{2} — (4)$$

Since  $1/g_{mp} \ll r_{dsn}$ ;  $\parallel$  comb gives  $1/g_{mp}$ .

All  $r_{ds}$  &  $g_m$  are same.

$$V_o' = \frac{g_m r_{ds} V_d}{4} — (5)$$

$$\text{Case 2) } V_o = -\frac{V_d}{2} ; V_o''$$

$$V_o'' = -g_m r_{ds} (r_{ds} || r_{dep}) (-V_d/2)$$

$$V_o'' = \frac{g_m r_{ds} V_d}{4} \quad \text{--- (6)}$$

Put (5) & (6) in (1)

$$\boxed{V_o = \frac{g_m r_{ds} V_d}{2}} \quad \text{--- (7)}$$

$$\boxed{K_d = \frac{V_o}{V_d} = \frac{g_m r_{ds}}{2}}$$

$$3) a) V_{DD} = 10V$$

$$m_n C_{ox} = 10^{-4} A/V^2$$

$$V_t = 1V.$$

$$I_{DS} = 0.5mA.$$

$$I_D = m_n C_{ox} \left(\frac{W}{L}\right) \frac{(V_{GS} - V_t)^2}{2}$$

$$0.5 \times 10^{-3} = 10^{-4} \times 1 \times \frac{(V_{GS} - 1)^2}{2}$$

$$V_{DS} = V_{GS}$$


$$V_{GS} = 4.16V$$

$$\boxed{V_{DS} = 4.16V}$$

$$V_{DD} - I_D R_D = V_{DS}$$

$$R_D = \frac{V_{DD} - V_{DS}}{I_D} = \frac{10 - 4.16}{0.5m}$$

$$\boxed{R_D = 11.68 k\Omega}$$

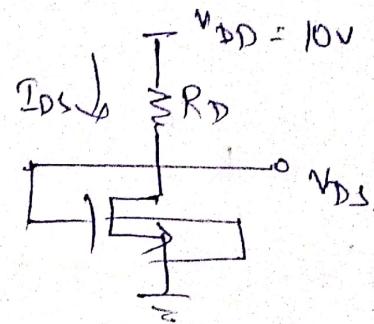

3b) From 1st stage

$$\frac{I_1}{1mA} = \frac{(w/l)_2}{(w/l)_1}$$

$$I_1 = \frac{3}{2} (1mA)$$

$$I_1 = 1.5mA$$

Since  $V_1 = 0$ , transistor 3 is off.  
Hence no current will flow from transistor 3 and 4.

$$I_1 = I_3 = 1mA$$

Now transistors 5 & 7 are matched.

$$I_3 \left(\frac{w}{l}\right)_7 = I_{out} \left(\frac{w}{l}\right)_5$$

$$(1.5)(40) = I_{out}(10)$$

$$I_{out} = \left(\frac{40}{10}\right)(1.5)$$

$$I_{out} = 6mA$$

$$c) (w/l)_{1,4} = 100, I_{SS} = 1mA, \lambda_n = 0.1, \lambda_p = 0.2$$



$$I_{SS} = 1mA$$

$$r_{dsn} = \frac{1}{\lambda_n \cdot \frac{I_{SS}}{2}} = \frac{1}{0.1 \times \frac{1mA}{2}}$$

$$r_{dsn} = 20k\Omega$$

$$r_{dsp} = \frac{1}{\lambda_p \cdot \frac{I_{SS}}{2}} = \frac{1}{0.2 \times \frac{1mA}{2}}$$

$$r_{dsp} = 10k\Omega$$

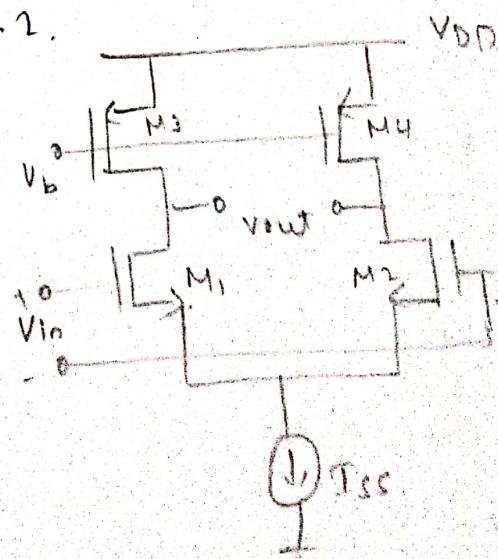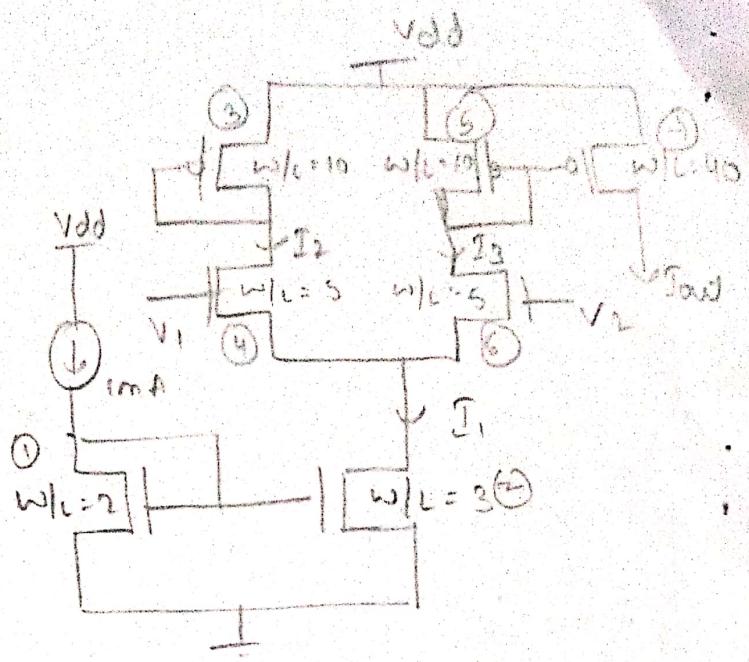

$$Ad_1 = \frac{g_m}{2 \left( \frac{1}{r_{dsn}} + \frac{1}{r_{dsp}} \right)}$$

$$g_{mni} = \sqrt{2 \mu_n C_{ox} (\omega_L) I_D}$$

$$= \sqrt{2 \times 134 \times 10^{-6} \times 100 \times 0.5 \times 10^{-3}}$$

$$= \sqrt{13.4 \times 10^{-6}}$$

$$g_{mD1} = 3.66 \times 10^{-3} V$$

$$\boxed{g_{m1} = 3.66 mV}$$

$$Ad_1 = \frac{3.66 mV}{\left( \frac{1}{20} + \frac{1}{10} \right)}$$

$$Ad_1 = 12.2$$

$$\therefore \text{Gain } Ad = Ad_2 - Ad_1 = 2Ad = 12.2 \times 2$$

$$\boxed{Ad = 24.4}$$

$$\rightarrow V_{out1, min} = V_{DG1} + V_{incm}$$

$$= V_{DS1} - V_{GS1} + V_{incm}$$

For  $V_{out}$  to be minimum,  $V_{DS1}$  should be minimum

$$V_{DS1, min} = V_{GS1} - V_t$$

$$\begin{aligned} V_{out, min} &= V_{incm} - V_t \\ &= 1.5 - 0.7 \end{aligned}$$

$$\boxed{V_{out, min} = 0.8 V}$$

$$V_{out, max} = V_{DD} - V_{S03}$$

For  $V_{out}$  to be max,  $V_{S03}$  should be minimum

$$V_{S03, min} = V_{SG3} - |V_{tp}|$$

$$\begin{aligned} V_{out, max} &= V_{DD} - V_{SG3} + |V_{tp}| \\ &= 3 - V_{SG} + 0.8 \end{aligned}$$

from current equation

$$V_{SG3} - 1V_{tp1} = \sqrt{\frac{2T_n}{ab\cos(\omega t)}} = \sqrt{\frac{2 \times 0.5 \times 10^{-3}}{38 \times 10^{-6} \times 102}}$$

$$V_{SG3} = 0.512 + 0.8$$

$$\boxed{V_{SG3} = 1.312 \text{ V}}$$

$$\boxed{V_{out, max} = 2.48 \text{ V}}$$




$$\text{output voltage swing} = 2(2.48 - 0.8)$$

$$= \boxed{3.36 \text{ V}}$$

## SCHOOL OF ELECTRONICS AND COMMUNICATION ENGINEERING

**Course Title:** Linear Integrated Circuits  
**Duration:** 75min  
**Max. Marks:** 40

**CourseCode:**19EECC203  
**Date:**27-05-2023  
**Time:**8.15am to 9.30pm

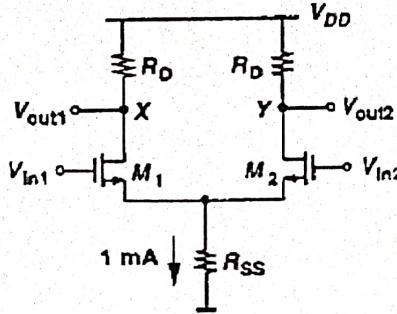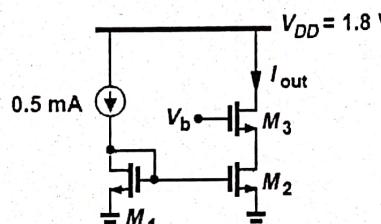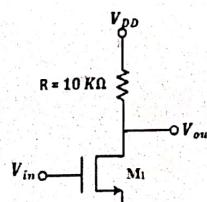Q. No	Note: Answer any two full questions	Marks
1a	<p>For the differential amplifier configuration given in Fig. Q1a, with <math>(W/L)_{1,2}=25/0.5</math>, <math>\mu_n C_{ox} = 50 \mu A/V^2</math>, <math>V_{TH} = 0.5V</math>, <math>\lambda = \gamma = 0</math> and <math>V_{DD} = 3V</math>. i) What is the required input CM for which <math>R_{SS}</math> sustains 0.6V? ii) Calculate <math>R_D</math> for a differential gain of 10</p> 	06
b	<p>Fig. Q1b depicts a cascode current source whose value is defined by the mirror arrangement, <math>M_1</math>-<math>M_2</math>. Assume <math>W/L = 5\mu m/0.18 \mu m</math> for <math>M_1</math>-<math>M_3</math>. Compute the value of <math>V_b</math> that <math>I_{out}</math> is precisely equal to 0.5 mA.</p> 	06
c	<p>With a neat circuit diagram of Widlar current mirror, explain and modify the circuit to increase the output resistance and derive the expression.</p>	08
2a	<p>For the MOSFET <math>M_1</math> shown in Fig.Q2a, assume <math>W/L=2</math>, <math>V_{DD}=2V</math>, <math>\mu_n C_{ox} = 100 \mu A/V^2</math> and <math>V_{TH}=0.5V</math>. Compute the value of <math>V_{in}</math> (volts) for which the transistor <math>M_1</math> switches from saturation region to linear region.</p> 	06
b.	<p>An integrated circuit employs the source follower and the common-source stage shown in Fig.Q2b. Design a current mirror that produces <math>I_1</math> and <math>I_2</math> from a 0.4mA reference.</p>	06

## SCHOOL OF ELECTRONICS AND COMMUNICATION ENGINEERING

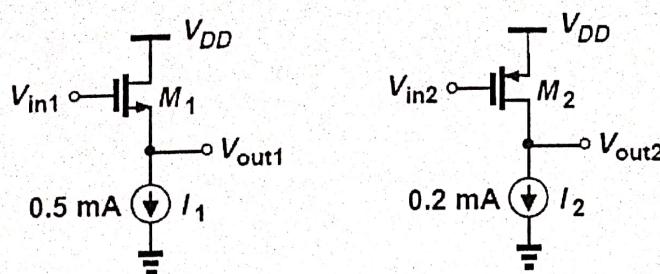


Fig.Q2b

c	Draw the circuit of 5 pack differential amplifier, explain and derive the equation for voltage gain.	08
3a	Given NMOS circuit as shown in Fig. Q3a, the specifications of the circuit are: $V_{DD} = 10V$ , $\mu_n C_{ox} = 10^{-4} A/V^2$ , $V_T = 1V$ and $I_{DS} = 0.5mA$ . Evaluate $V_{DS}$ and $R_D$ . Neglect body effect.	06
	Fig.Q3a	
b	In the circuit shown in Fig.Q3b, $V_1=0V$ and $V_2=V_{dd}$ . The relevant parameters are mentioned in the Fig. Q3b. Ignoring the effect of channel length modulation and body effect, Compute the $I_{out}$	06
	Fig.Q3b	
c	For the circuit shown in Fig. Q3c, ( $W/L$ ) 1-4 = $50/0.5$ , $ISS=1mA$ , $\lambda n=0.1$ and $\lambda p=0.2$ , what is the small signal differential gain? For $V_{in,CM}=1.5V$ , What is maximum allowable output voltage swing?	08
	Fig.Q3c	